

Lab 5 Report

Part 1 – Ripple Carry Adder (RCA)

i. Design Files for RCA

a. RCA_4bits

```
module RCA_4bits(  
    input clk,  
    input enable,  
    input [3:0] A, B,  
    input Cin,  
    output [4:0] Q  
);  
  
    wire c1, c2, c3;  
    wire [4:0] Data;  
  
    full_adder FA1 (A[0], B[0], Cin, Data[0], c1),  
                FA2 (A[1], B[1], c1, Data[1], c2),  
                FA3 (A[2], B[2], c2, Data[2], c3),  
                FA4 (A[3], B[3], c3, Data[3], Data[4]);  
  
    register_logic r1(clk, enable, Data, Q);  
endmodule
```

b. full_adder

```
module full_adder(  
    input A, B, Cin,  
    output S, Cout  
);  
    wire s1, c1, c2;  
  
    xor (S, A, B, Cin);  
    or (Cout, B & Cin, A & Cin, A & B);  
endmodule
```

c. register_logic

```
module register_logic(  
    input clk,  
    input enable,  
    input [4:0] Data,  
    output reg [4:0] Q  
);  
  
    initial begin  
        Q = 4'b0000;  
    end  
  
    always @(posedge clk) begin  
        if(enable)  
            Q = Data;  
    end  
endmodule
```

ii. Test-bench for RCA

```

module tb_RCA_4bits;

    reg clk;
    reg enable;
    reg [3:0] A;
    reg [3:0] B;
    reg Cin;

    wire [4:0] Q;

    RCA_4bits uut (
        .clk(clk),
        .enable(enable),
        .A(A),
        .B(B),
        .Cin(Cin),
        .Q(Q)
    );

    initial begin

        // Initialization
        clk = 0;
        enable = 1;
        A = 0;
        B = 0;
        Cin = 0;

        #10;

        // Test Case 1
        A = 4'b0001;
        B = 4'b0101;
        Cin = 1'b0;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 2
        A = 4'b0111;
        B = 4'b0111;
        Cin = 1'b0;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 3
        A = 4'b1000;
        B = 4'b0111;
        Cin = 1'b1;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 4
        A = 4'b1100;
        B = 4'b0100;
        Cin = 1'b0;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 5
        A = 4'b1000;
        B = 4'b1000;
        Cin = 1'b01;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 6
        A = 4'b1001;
        B = 4'b1010;
        Cin = 1'b1;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 7
        A = 4'b1111;
        B = 4'b1111;
        Cin = 1'b0;
        enable = 1;

        #10;

        enable = 0;

        #10;

        clk = 0;
        enable = 1;
        A = 0;
        B = 0;
        Cin = 0;

        #10;

        end

        always
            #5 clk = ~clk;

    endmodule

```

iii. Testcases Table for RCA

A[3:0]	B[3:0]	Cin	Sum[3:0]	Cout
0001	0101	0	0110	0
0111	0111	0	1110	0
1000	0111	1	0000	1
1100	0100	0	0000	1
1000	1000	1	0001	1
1001	1010	1	0100	1
1111	1111	0	1110	1

iv. Constraints File for RCA


```
## Clock signal
set_property PACKAGE_PIN W5 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk]

## Switches
set_property PACKAGE_PIN V17 [get_ports {A[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[0]}]
set_property PACKAGE_PIN V16 [get_ports {A[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[1]}]
set_property PACKAGE_PIN W16 [get_ports {A[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[2]}]
set_property PACKAGE_PIN W17 [get_ports {A[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[3]}]
set_property PACKAGE_PIN W15 [get_ports {B[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[0]}]
set_property PACKAGE_PIN V15 [get_ports {B[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[1]}]
set_property PACKAGE_PIN W14 [get_ports {B[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[2]}]
set_property PACKAGE_PIN W13 [get_ports {B[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[3]}]
set_property PACKAGE_PIN V2 [get_ports {Cin}]
set_property IOSTANDARD LVCMOS33 [get_ports {Cin}]

## LEDs
set_property PACKAGE_PIN U16 [get_ports {Q[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[0]}]
set_property PACKAGE_PIN E19 [get_ports {Q[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[1]}]
set_property PACKAGE_PIN U19 [get_ports {Q[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[2]}]
set_property PACKAGE_PIN V19 [get_ports {Q[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[3]}]
set_property PACKAGE_PIN W18 [get_ports {Q[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[4]}]

##Buttons
set_property PACKAGE_PIN U18 [get_ports enable]
set_property IOSTANDARD LVCMOS33 [get_ports enable]
```

v. Simulation Waveform for RCA TB

 

Part 2 – Carry Lookahead Adder (CLA)

vi. C_i and S_i Equations

$$C_0 = C_{in}$$

$$C_1 = P_0 C_0 + G_0$$

$$C_2 = P_1 P_0 C_0 + P_1 G_0 + G_1$$

$$C_3 = P_2 P_1 P_0 C_0 + P_2 P_1 G_0 + P_2 G_1 + G_2$$

$$C_4 = C_{out} = P_3 P_2 P_1 P_0 C_0 + P_3 P_2 P_1 G_0 + P_3 P_2 G_1 + P_3 G_2 + G_3$$

$$S_0 = P_0 \oplus C_0$$

$$S_1 = P_1 \oplus C_1$$

$$S_2 = P_2 \oplus C_2$$

$$S_3 = P_3 \oplus C_3$$

vii. Design Files for CLA

a. CLA_4bits

```
module CLA_4bits(  
    input clk,  
    input enable,  
    input [3:0] A, B,  
    input Cin,  
    output [4:0] Q  
);  
  
    wire [3:0] G, P, S;  
    wire [4:0] C, Data;  
    wire Cout;  
  
    assign G = A & B;  
    assign P = A ^ B;  
    assign C[0] = Cin;  
    assign C[1] = G[0] | (P[0] & C[0]);  
    assign C[2] = G[1] | (P[1] & G[0]) | (P[1] & P[0] & C[0]);  
    assign C[3] = G[2] | (P[2] & G[1]) | (P[2] & P[1] & G[0]) | (P[2] & P[1] & P[0] & C[0]);  
    assign Cout = G[3] | (P[3] & G[2]) | (P[3] & P[2] & G[1]) | (P[3] & P[2] & P[1] & G[0])  
                | (P[3] & P[2] & P[1] & P[0] & C[0]);  
    assign S = P ^ C;  
  
    assign Data = {Cout, S};  
  
    register_logic r1(clk, enable, Data, Q);  
endmodule
```

b. register_logic

```
module register_logic(  
    input clk,  
    input enable,  
    input [4:0] Data,  
    output reg [4:0] Q  
);  
  
    initial begin  
        Q = 4'b0000;  
    end  
  
    always @(posedge clk) begin  
        if(enable)  
            Q = Data;  
    end  
endmodule
```

viii. Test-bench for CLA

```
module tb_CLA_4bits;

    reg clk;
    reg enable;
    reg [3:0] A;
    reg [3:0] B;
    reg Cin;

    wire [4:0] Q;

    CLA_4bits uut (
        .clk(clk),
        .enable(enable),
        .A(A),
        .B(B),
        .Cin(Cin),
        .Q(Q)
    );

    initial begin

        // Initialization
        clk = 0;
        enable = 1;
        A = 0;
        B = 0;
        Cin = 0;

        #10;

        // Test Case 1
        A = 4'b0000;
        B = 4'b0101;
        Cin = 1'b0;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 2
        A = 4'b0101;
        B = 4'b0111;
        Cin = 1'b0;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 3
        A = 4'b1000;
        B = 4'b0111;
        Cin = 1'b1;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 4
        A = 4'b1001;
        B = 4'b0100;
        Cin = 1'b0;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 5
        A = 4'b1000;
        B = 4'b1000;
        Cin = 1'b1;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 6
        A = 4'b1101;
        B = 4'b1010;
        Cin = 1'b1;
        enable = 1;

        #10;

        enable = 0;

        #10;

        // Test Case 7
        A = 4'b1110;
        B = 4'b1111;
        Cin = 1'b0;
        enable = 1;

        #10;

        enable = 0;

        #10;

        clk = 0;
        enable = 1;
        A = 0;
        B = 0;
        Cin = 0;

        end

        always
            #5 clk = ~clk;

    endmodule
```

ix. Testcases Table for CLA

A[3:0]	B[3:0]	Cin	Sum[3:0]	Cout
0000	0101	0	0101	0
0101	0111	0	1100	0
1000	0111	1	0000	1
1001	0100	0	1101	0
1000	1000	1	0001	1
1101	1010	1	1000	1
1110	1111	0	1101	1

x. Constraints File for CLA


```
## Clock signal
set_property PACKAGE_PIN W5 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk]

## Switches
set_property PACKAGE_PIN V17 [get_ports {A[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[0]}]
set_property PACKAGE_PIN V16 [get_ports {A[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[1]}]
set_property PACKAGE_PIN W16 [get_ports {A[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[2]}]
set_property PACKAGE_PIN W17 [get_ports {A[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[3]}]
set_property PACKAGE_PIN W15 [get_ports {B[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[0]}]
set_property PACKAGE_PIN V15 [get_ports {B[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[1]}]
set_property PACKAGE_PIN W14 [get_ports {B[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[2]}]
set_property PACKAGE_PIN W13 [get_ports {B[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[3]}]
set_property PACKAGE_PIN V2 [get_ports {Cin}]
set_property IOSTANDARD LVCMOS33 [get_ports {Cin}]

## LEDs
set_property PACKAGE_PIN U16 [get_ports {Q[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[0]}]
set_property PACKAGE_PIN E19 [get_ports {Q[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[1]}]
set_property PACKAGE_PIN U19 [get_ports {Q[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[2]}]
set_property PACKAGE_PIN V19 [get_ports {Q[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[3]}]
set_property PACKAGE_PIN W18 [get_ports {Q[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[4]}]

##Buttons
set_property PACKAGE_PIN U18 [get_ports enable]
set_property IOSTANDARD LVCMOS33 [get_ports enable]
```


xi. Simulation Waveform for CLA TB

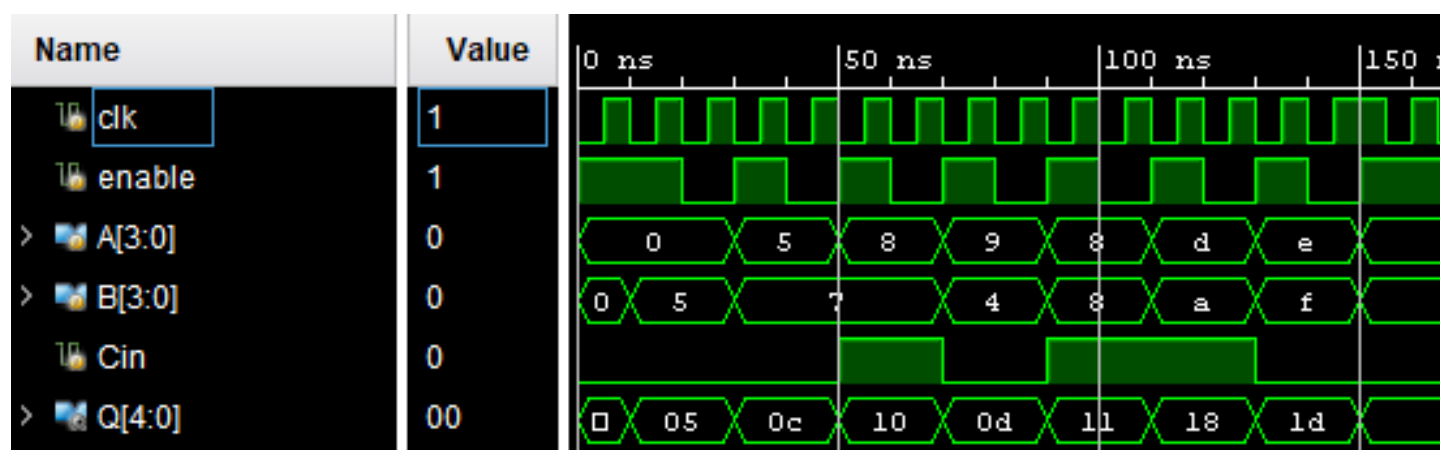


Part 3 – Speed and Area Comparison of RCA vs. CLA

xii. Screenshots of Gate-Level Schematics

a. RCA

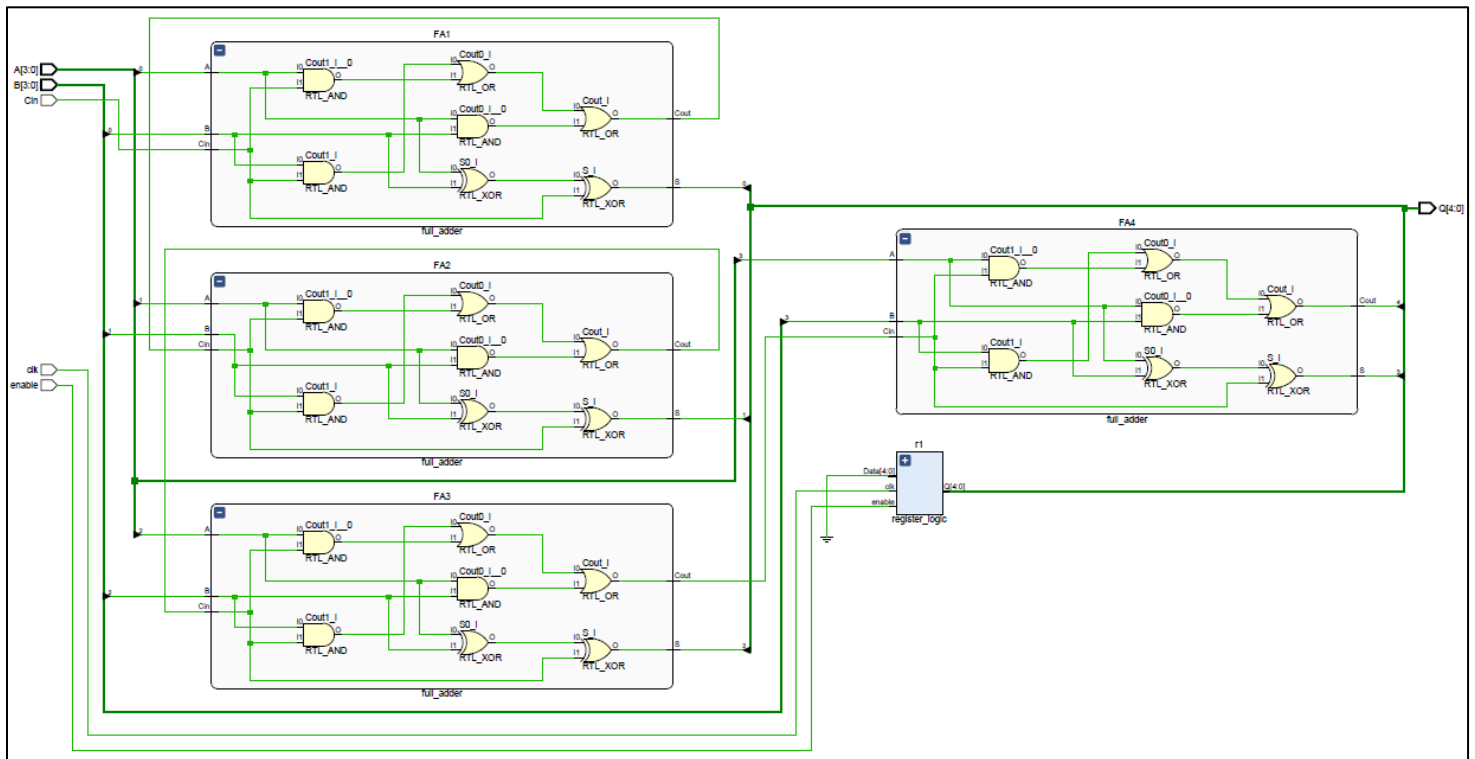

b. CLA

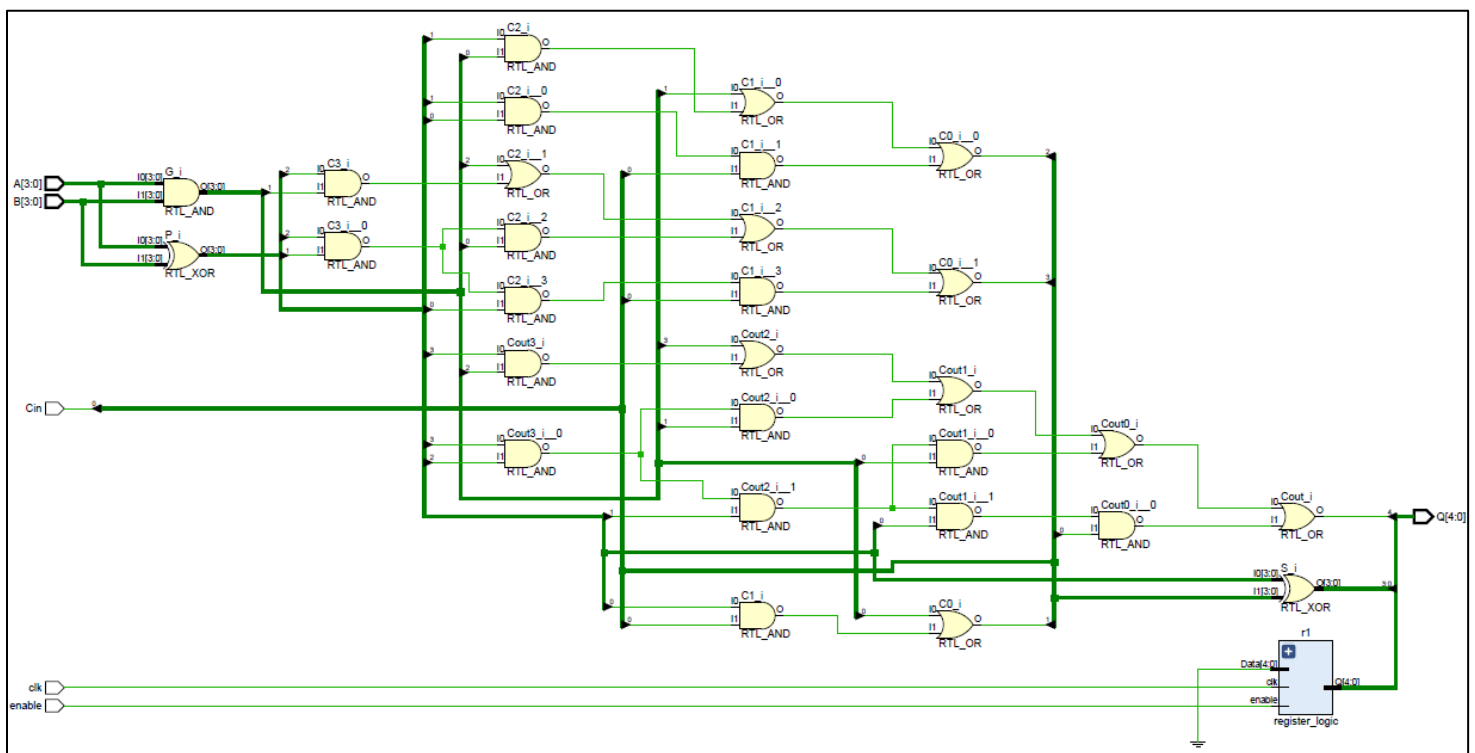

xiii. Delay and Area Calculations

a. RCA

There are 4 full adders each with 3 AND, 2 OR, and 2 XOR gates. The areas for these gates are 4, 4, and 6 respectively. This means the total area comes for the equation: $4(3(4) + 2(4) + 2(6)) = 4(32) = 128$ units of area.

The critical path through our full adder design is the C_{out} path for each full adder. This means going through an AND gate, then 2 OR gates. The time take for each full adder is $3 + 2(2) = 7ns$, this multiplied by 4 since there are 4 full adders to go through means the critical path would take $28ns$.

b. CLA

My CLA design has 20 AND, 10 OR, and 8 XOR gates. Multiplied by their areas this gives us the following equation: $20(4) + 10(4) + 8(6) = 168$ units of area.

The critical path through the carry adder is through 1 XOR, 4 AND, and 2 OR gates. This gives us the following time equation $1(3) + 4(3) + 2(2) = 19ns$.

xiv. RCA and CLA Delay and Area Analysis

The RCA design has a smaller area footprint but takes a lot longer than the CLA design. The CLA design has the converse, with a larger area but a lesser critical path. This means in space constrained design I would implement the RCA, but in a time constrained design I would implement the CLA.